

## **BMC018. Analog Drum.**

Last updated 12-27-2020

### **I Features**

### **II Schematics**

- A.Master Schematic.**
- B.Input/Decay**
- C.VCO**
- D.VCA**
- E.Power Connections.**

### **III Construction**

- A.Parts List**
- B.The Board**

## **I. Features**


This module is an analog drum sound. It was designed to be built using a minimum of parts and no difficult to obtain parts. I initially was only trying to build a "disco tom" type sound, but I'm more impressed with it's bass-drum like sounds. It has the following controls:

1. Amplitude Decay
2. Frequency Modulation Decay
3. Depth of Frequency Decay
4. Baseline frequency
5. External Frequency CV Depth

It has just two inputs, one for a trigger and one for external CV.
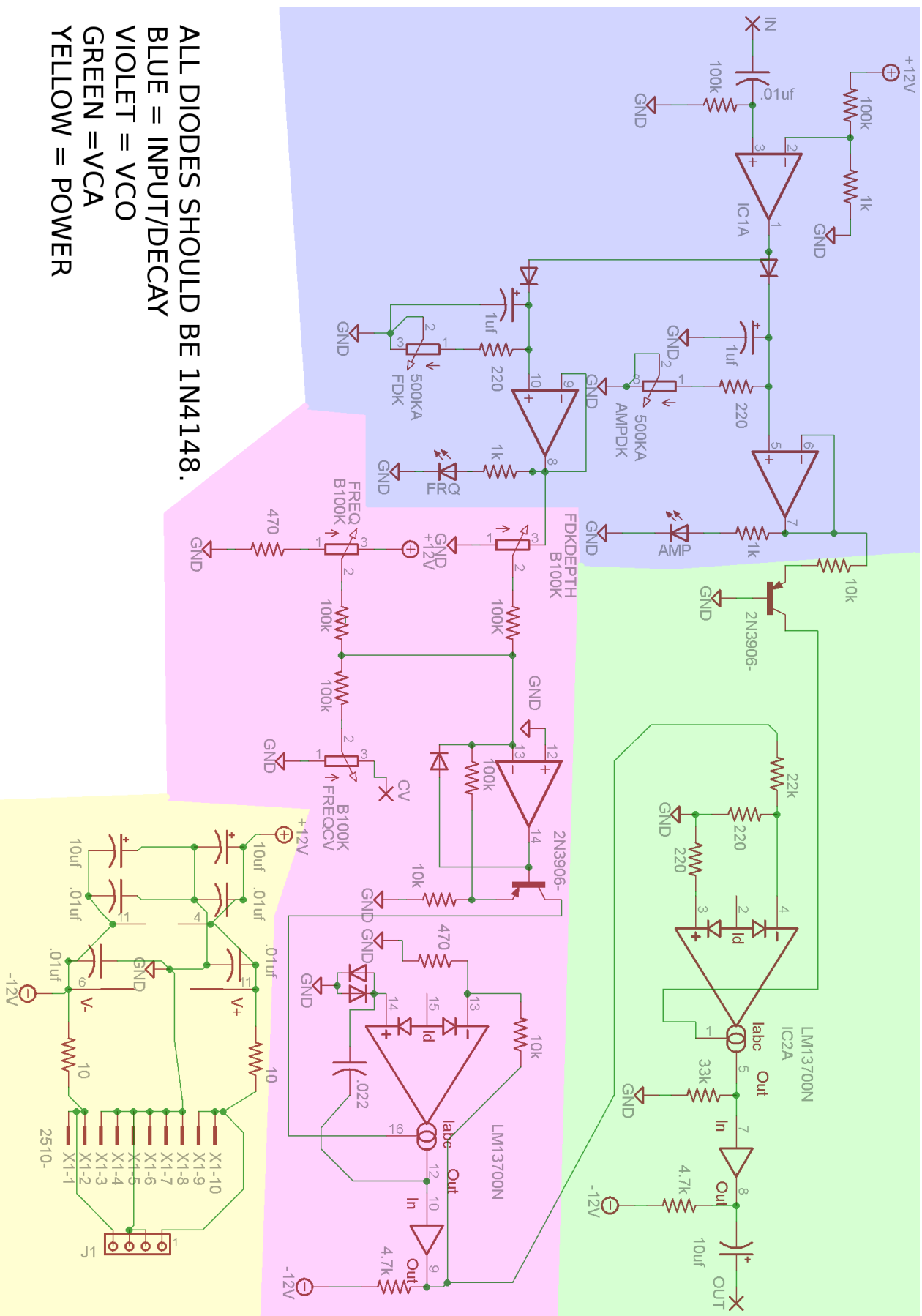
## **II. Schematics.**

On the next page is the master schematic. There are highlighted sections of the master schematic that indicate what sub-circuit of the module the parts correspond to, these sub-circuits are then described on the following pages.





## INPUT/DECAY

On the far left we see the wirepad marked "IN." A trigger or gate signal should be input here. The .01uF capacitor and 100K resistor to ground form a pulse shortener, making the pulse length of the input signal irrelevant. This is then input to an op-amp wired as a comparator. The output of the comparator goes to the two decay sections through a pair of 1N4148 diodes.

When the output goes high, current flows through these diodes quickly charging the 1uF capacitors. The 220 ohm resistors and 500KA pots in parallel with the capacitors provide a path for the capacitors to discharge the voltage. The higher the resistance, the more slowly the capacitors discharge.

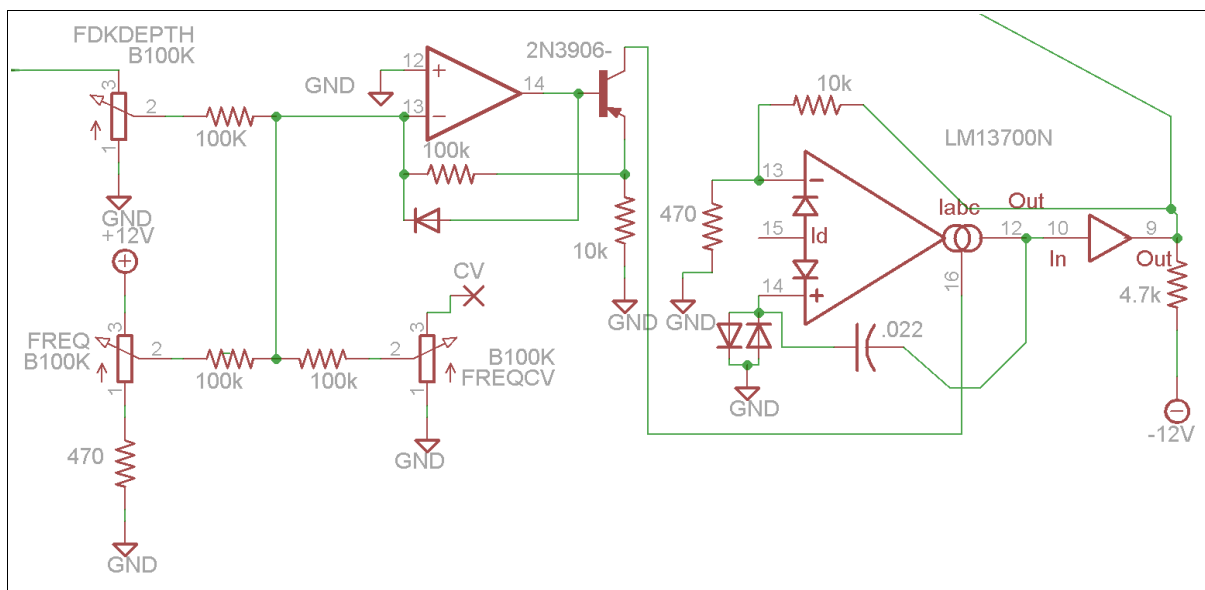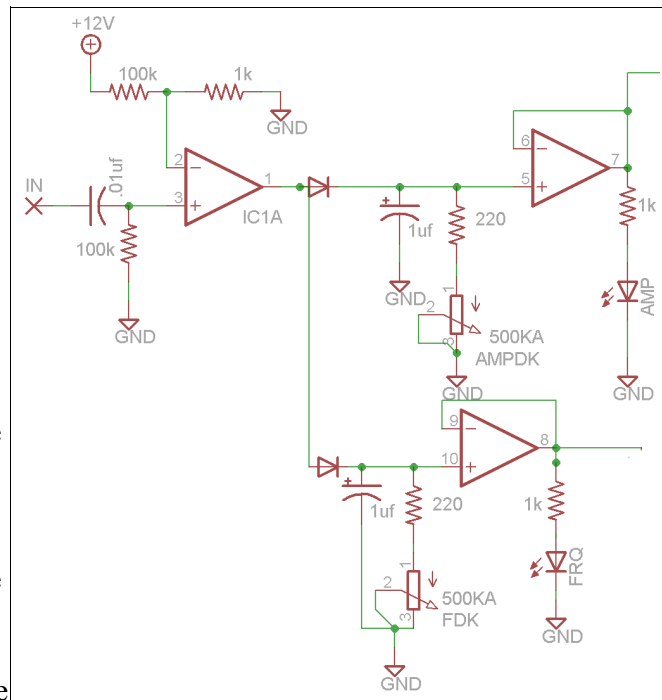Each capacitor is also connected to an op-amp wired as a buffer, which is outputting the capacitor's voltage onto the next stage, as well as lighting up an LED indicator. The output of the Frequency Decay section goes to the VCO, and the output of the Amplitude Decay section goes to the VCA.




## VCO

On the far left we see the input from the decay circuit. This voltage is summed with the voltages from the external frequency control and the baseline frequency control. These voltages are summed together on the negative input of the op amp wired in conjunction with a 2N3906 to form a linear voltage controlled current source.

This current source is controlling the current of one half of an LM13700 OTA wired as a VCO. The design for the VCO is taken from the LM13700 datasheet. The OTA is forming an Integrator/Schmitt Trigger type oscillator by itself.

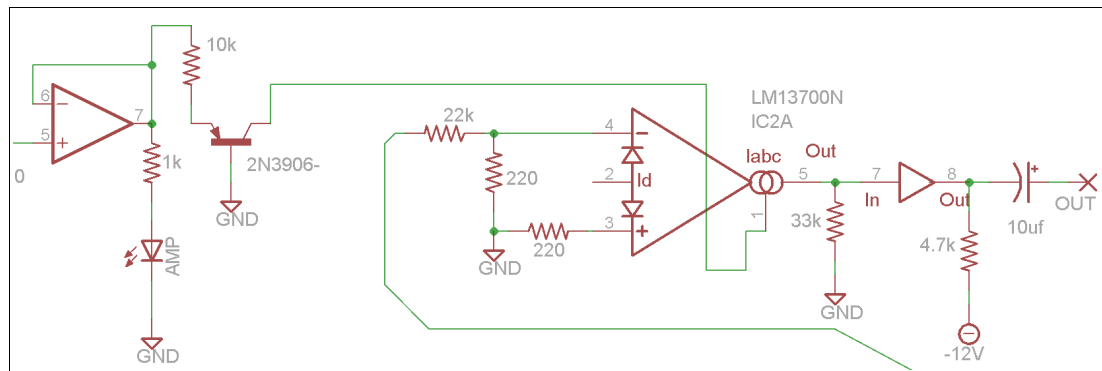**IF BUILDING FOR +/-15V** replace the 10K resistor in the feedback path of the OTA with a 15K. This is untested, if it works for you, or you like it more with a different value, let me know!




## VCA

On the far left we see the output of the decay section for amplitude. A single 2n3906 in series with a 10k resistor forms the current control. This VCA is incredibly simple, the signal is input to the inverting input through a 22K and 220 ohm resistor voltage divider used to limit the signal on the input. The output of the VCA goes through the onboard buffer and then a 10uf capacitor to decouple the DC bias.
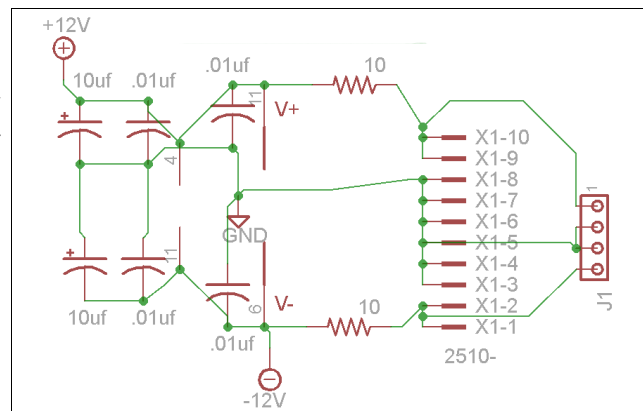
## Power Connections.

Here we see the two power connectors for MOTM and Eurorack style systems. The supply is filtered by a 10 ohm resistor and 10uf capacitor, and then .01uf decoupling capacitors are placed near the power supply pins of the two ICs.



## Parts List

### Semiconductors

Value	Qty	Notes
TL074	1	
LM13700	1	or 13600
2N3906	2	
1N4148	5	
LED	2	3mm

### Resistors

Value	Qty	Notes
10 ohm	2	7.5mm lead spacing
220 ohm	4	" "
470 ohm	2	" "
1K ohm	3	" "
4.7K	2	" "
10K	3	" "
22K	1	" "
33K	1	" "
100K	6	" "
500KA Potentiometer	2	16mm pot, PCB mounted
100KB Potentiometer	3	" "


### Capacitors

Value	Qty	Notes
.01uf	5	cheap ceramic 2.54mm
0.022uf	1	Poly 5mm lead spacing
1uf	2	Electrolytic
10uf	3	" "

### Other

Value	Qty	Notes
Power Connector	1	Either Eurorack or MOTM
14pin DIP Socket	1	
16pin DIP socket	1	

Jacks	3	Either 1/4" or 1/8"
Knobs	5	

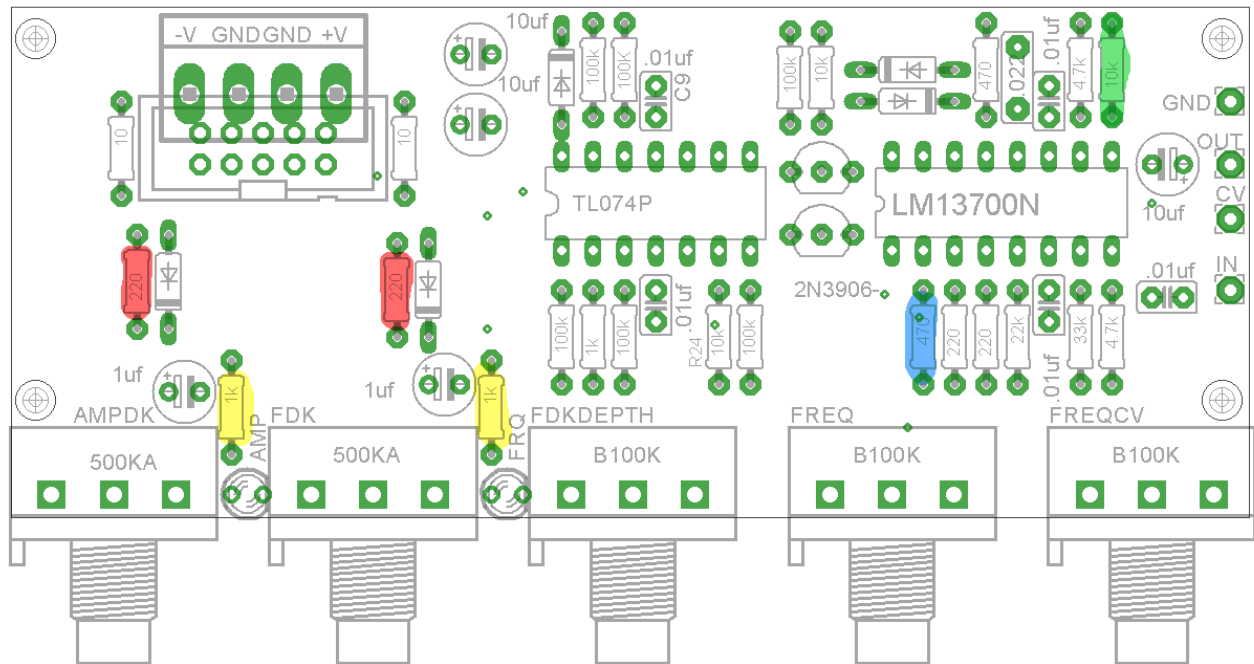

## The Board

The PCB is 100mm x 41mm. The pots are spaced 21mm apart. The mounting holes are spaced 91mm x 29mm.

I've highlighted a few key resistors that a builder may want to modify.

The yellow resistors control the brightness of the LEDs. 1K is appropriate for normal Red, Green or Yellow LEDs. For high efficiency LEDs of these colors or blue/white LEDs try changing to 10K.

The red resistors control the minimum decay time. To increase the minimum time, increase the value of the resistor. If you have a problem where when turning one of the decay pot times down all the way where the decay controlled by the other pot is also shortened, you should increase the value of these resistors.

The blue resistor controls the minimum frequency on the frequency control pot. Increase it to increase the minimum frequency.

The green resistor is the 10K that should be replaced with a 15K for +/-15V

## WIRING

The PCB has four wirepads, they should be connected as follows:


IN → Tip of the Trigger/Gate Input Jack

CV → Tip of the CV Input Jack

OUT → Tip of the Output jack, and optionally the switch of the CV jack.

GND → The sleeve of any one jack if using a metal panel. If using a non-conductive panel, then connect the sleeves of the jacks together.

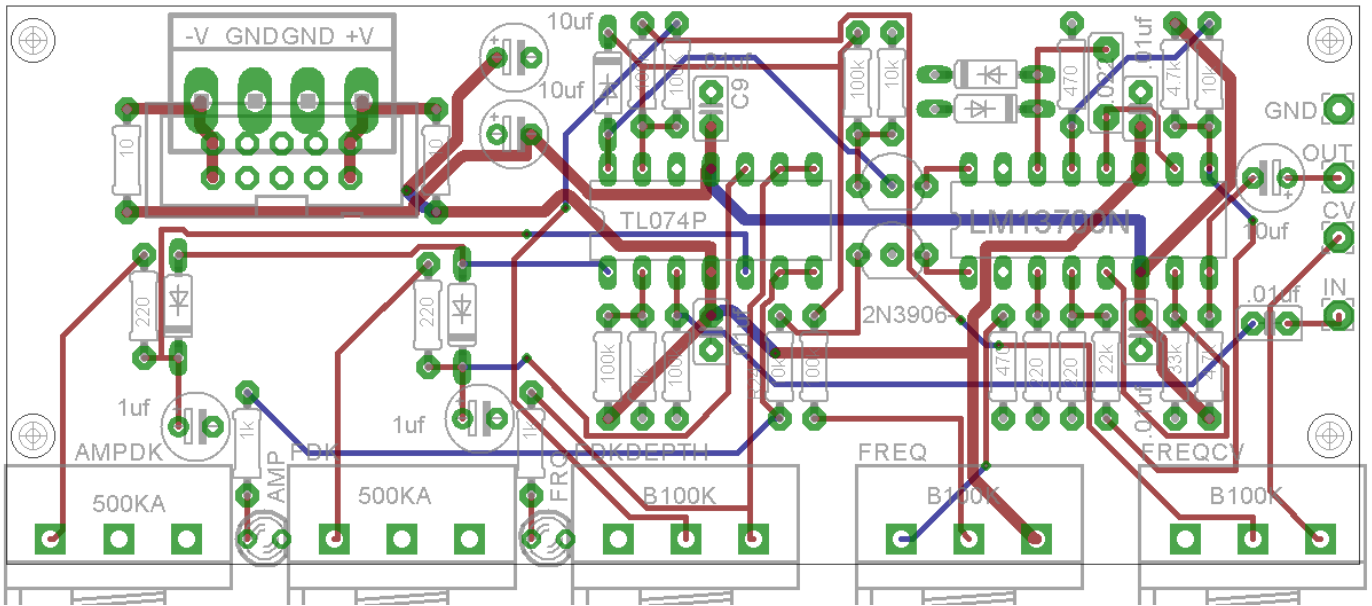Below is an image of the PCB with traces included to help when troubleshooting. The ground plane is not depicted, so assume pads with no connection are connected to ground:



## Installing LEDs Sideways

The PCB indicates that the LEDs should be mounted parallel to the board, do not do this. Leds should be pointing in the same direction as the pots. The leads of the LED should be bent at a 90 degree angle, the easiest way to install them is in four steps:

1. Place the LED on the edge of the board facing out with it's leads going over it's pads on the PCB. Make sure the bottom lip of the LED is flush with the board.
2. Clip the leads 2 or 3 mm past the pads on the PCB.
3. Bend the LED leads 90 degrees 2 or 3mm from the edge.
4. The LED should pop into place easily.

